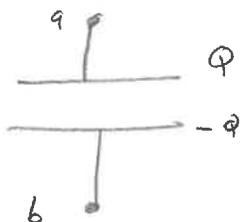


Chapter 26

1



$\Delta V$  between a and b = 12 volt

$Q = 12 \mu C$


a)  $Q = C \Delta V \rightarrow C = \frac{Q}{\Delta V} = \frac{12 \mu C}{12 \text{ Volt}} = 1 \mu \text{ Farad}$

b) Assume now that  $Q = 144 \mu C$

$\Delta V = \frac{Q}{C} = \frac{144 \mu C}{1 \mu \text{ Farad}} = 144 \text{ volts}$

so potential difference increases by the same factor as the increase in charge

2

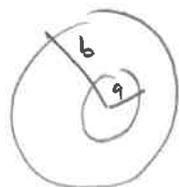

air-filled ( $k=1$ )  
spherical capacitor

$a = 7.10 \text{ cm}$


$b = 13.2 \text{ cm}$

a)  $C = 4\pi\epsilon_0 \left(\frac{ab}{b-a}\right) = 1.7 \times 10^{-11} \text{ Farad} = 17 \text{ pF} \quad (1 \text{ pF} = 10^{-12} \text{ Farad})$

b)  $Q = 4 \mu C$

$\Delta V = \frac{Q}{C} = \frac{4 \times 10^{-6} \text{ C}}{1.7 \times 10^{-12} \text{ F}} = 0.234 \times 10^6 \text{ volts} = 234 \text{ kV}$

3

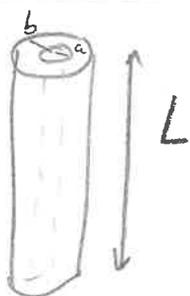

$L = 45 \text{ m}$ ,

(air-filled so  $k=1$ )

$a = \text{inner radius} = 2.58 \text{ mm}$

$b = \text{outer radius} = \frac{7.27 \text{ mm}}{2}$

$Q = 8.10 \mu C$

a)  $C = \frac{2\pi\epsilon_0 L}{\ln(b/a)} = 2.42 \times 10^{-9} \text{ C} = 2.42 \text{ nF}$

b)  $\Delta V = \frac{Q}{C} = 3.35 \text{ kV}$

(4.)

air filled:  $\epsilon_0 = 1$ 

$$A = 2,10 \text{ cm}^2 \left(\frac{\text{m}}{100\text{cm}}\right)^2 = 2,10 \times 10^{-4} \text{ m}^2$$

$$d = 1 \text{ mm}$$


$$\Delta V = 9 \text{ V}$$

$$a) C = \frac{\epsilon_0 A}{d} = 1,86 \times 10^{-12} \text{ F} = \boxed{1,86 \text{ pF}}$$

$$b) Q = C \Delta V = 1,86 \times 10^{-12} \text{ F} \cdot 9 \text{ volts} = \boxed{16,7 \text{ pC}}$$

$$c) |E| = \frac{\Delta V}{d} = \frac{9 \text{ V}}{1 \text{ mm}} = \boxed{9000 \frac{\text{V}}{\text{m}}}$$

(5.)

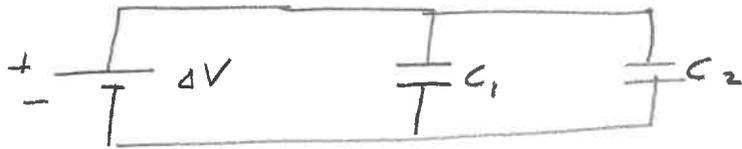

$$C_1 = 6 \mu\text{F}$$

$$C_2 = 13 \mu\text{F}$$

$$\Delta V = 9 \text{ V}$$


$$a) C_{eq} = C_1 + C_2 = \boxed{19 \mu\text{F}}$$

$$b) \Delta V_1 = \Delta V = \boxed{9 \text{ volts}}, \quad \Delta V_2 = \Delta V = \boxed{9 \text{ volts}}$$

$$c) Q_1 = C_1 \Delta V_1 = 6 \mu\text{F} \cdot 9 \text{ volts} = \boxed{54 \mu\text{C}}$$

$$Q_2 = C_2 \Delta V_2 = 13 \mu\text{F} \cdot 9 \text{ volts} = \boxed{117 \mu\text{C}}$$

(6.)

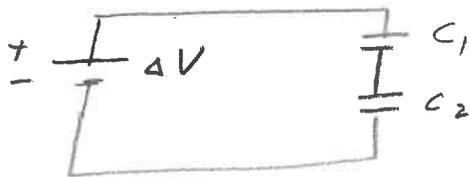

$$C_1 = 3 \mu\text{F}$$

$$C_2 = 16 \mu\text{F}$$

$$\Delta V = 9 \text{ volt}$$

$$a) C_{eq} = \frac{1}{\frac{1}{C_1} + \frac{1}{C_2}} = \boxed{2,52 \mu\text{F}}$$



$$b) Q = C_{eq} \Delta V = 22,7 \mu\text{C}$$


This  $Q$  is on each of  $C_1$  and  $C_2$

$$\text{Thus, } \Delta V_1 = \frac{Q}{C_1} = \boxed{7,58 \text{ volts}}$$

$$\Delta V_2 = \frac{Q}{C_2} = \boxed{1,42 \text{ volts}}$$

$$c) Q_1 = \boxed{22,7 \mu\text{C}}, \quad Q_2 = \boxed{22,7 \mu\text{C}}$$

(7)

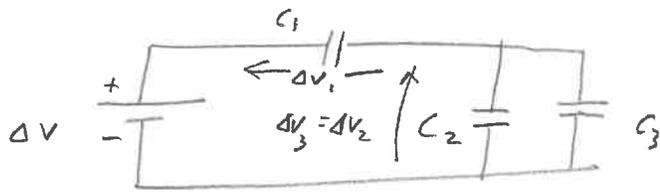

$$\begin{aligned} C_1 &= 3C \\ C_2 &= C \\ C_3 &= 5C \end{aligned}$$

$$\equiv \Delta V + \left[ \text{Circuit with } C_1 \text{ in series with } C_p = C_2 + C_3 \right] \quad (P: \text{parallel})$$

$$\equiv \Delta V + \left[ \text{Circuit with } C_{eq} \right] \quad C_{eq} = \frac{1}{\frac{1}{C_1} + \frac{1}{C_p}} = \frac{1}{\frac{1}{3C} + \frac{1}{6C}}$$

$$\begin{aligned} a) \quad C_p &= C_2 + C_3 = C + 5C = 6C \\ C_{eq} &= \frac{1}{\frac{1}{3C} + \frac{1}{6C}} = \frac{C}{\left(\frac{1}{3} + \frac{1}{6}\right)} = \boxed{2C} \end{aligned}$$

$$b) \quad Q_{eq} = C_{eq} \Delta V = 2C \Delta V$$

This is charge on  $C_1$  and  $C_p = C_2 + C_3$

$$\text{so } Q_1 = Q_{eq} = (2C) \Delta V = C_1 \Delta V_1$$

$$Q_p = Q_{eq} = Q_2 + Q_3 = C_2 \Delta V_2 + C_3 \Delta V_3 = (C_2 + C_3) \Delta V_p$$

$$\text{where } \Delta V = \Delta V_1 + \Delta V_p$$

$$\text{so } \begin{cases} Q_1 = Q_2 + Q_3 (= Q_{eq}) \\ Q_2 = C_2 \Delta V_p = C \Delta V_p \\ Q_3 = C_3 \Delta V_p = 5C \Delta V_p \end{cases} \Rightarrow Q_1 > Q_3 > Q_2$$

c) potential differences

$$\Delta V_1 = \frac{Q_1}{C_1} = \frac{Q_{eq}}{3C} = \frac{2C \Delta V}{3C} = \boxed{\frac{2}{3} \Delta V}$$

$$\Delta V_2 = \Delta V_3 = \Delta V_p = \frac{Q_p}{C_p} = \frac{Q_{eq}}{6C} = \frac{2C \Delta V}{6C} = \boxed{\frac{1}{3} \Delta V}$$

$$\text{thus } \boxed{\Delta V_1 > \Delta V_2 = \Delta V_3}$$

$$d) \text{ IF } C_3 \uparrow \text{ then } C_p \uparrow \Rightarrow C_{eq} \uparrow \Rightarrow Q_{eq} \uparrow \Rightarrow \boxed{Q_1 \uparrow}$$


$$\Rightarrow \Delta V_1 \uparrow \Rightarrow \Delta V_2 = \Delta V_3 \downarrow \Rightarrow \boxed{Q_2 \downarrow} \Rightarrow \boxed{Q_3 \uparrow}$$

$$\text{since } Q_3 = Q_1 - Q_2$$

(3)

(8.)

a)

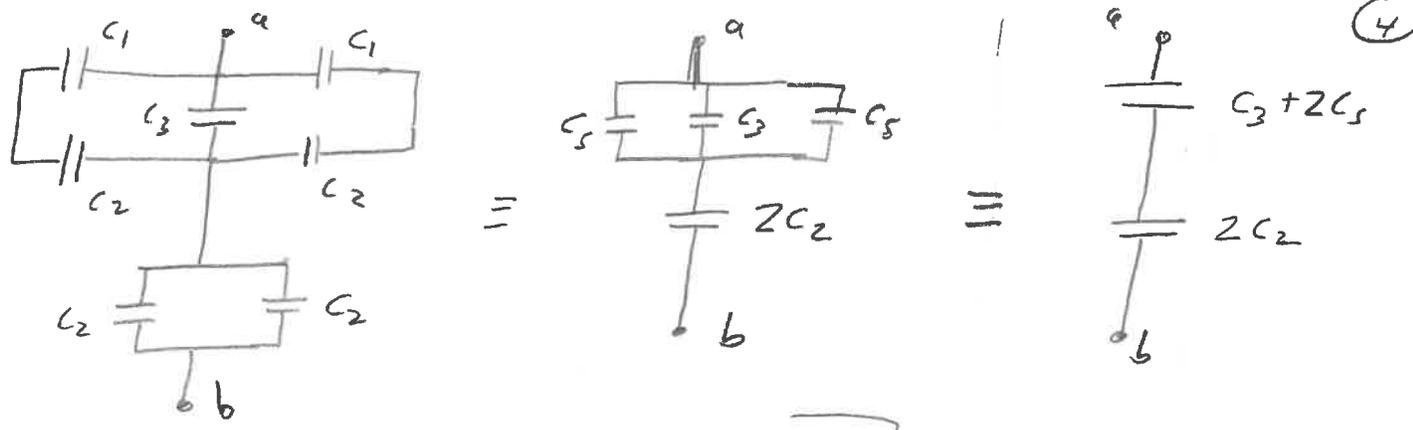

where  $C_s = \frac{1}{\frac{1}{C_1} + \frac{1}{C_2}} = \frac{C_1 C_2}{C_1 + C_2} = 4.1 \mu F$

$\equiv$

$$C_{eq} = \frac{1}{\frac{1}{C_3 + 2C_s} + \frac{1}{2C_2}}$$

$$= \frac{1}{\frac{1}{C_3 + \left(\frac{2C_1 C_2}{C_1 + C_2}\right)} + \frac{1}{2C_2}}$$

$$= \boxed{7.8 \mu F}$$


Assume  $C_1 = 6 \mu F$   
 $C_2 = 13 \mu F$   
 $C_3 = 3 \mu F$

b)

$\Delta V = 60 V$   
 $Q_{eq} = C_{eq} \Delta V$

$\Delta V_{top} = \frac{Q_{eq}}{C_{top}} = \frac{C_{eq} \Delta V}{C_{top}}$

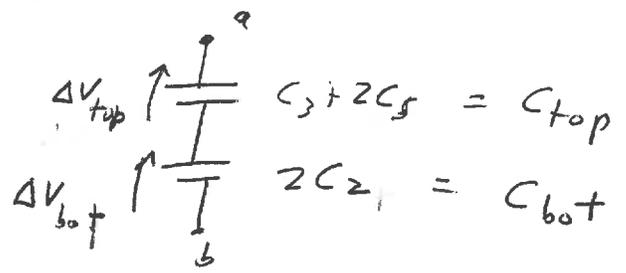
$\Delta V_{bot} = \frac{Q_{eq}}{C_{bot}} = \frac{C_{eq} \Delta V}{C_{bot}}$



thus,  $\Delta V_{top} = 41.9 V$  ,  $\Delta V_{bot} = 18.1 V$

$\rightarrow Q_3 = C_3 \Delta V_{top} = \boxed{126 \mu C}$


(9.)

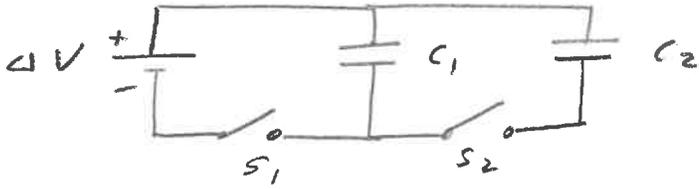

$C_1 = 8 \mu F$   
 $C_2 = 9 \mu F$   
 $\Delta V = 22 V$

(5)

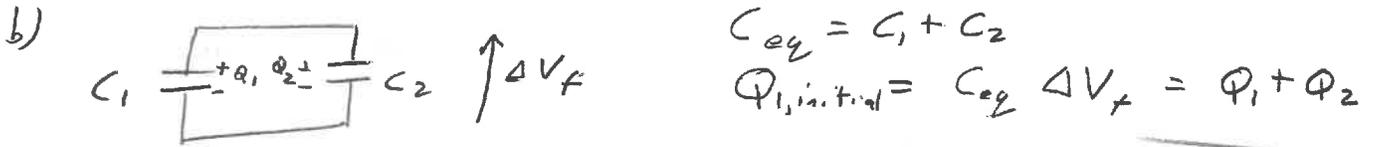a)  $Q_{1, initial} = C_1 \Delta V = 8 \mu F \cdot 22 V = \boxed{176 \mu C}$  (initial charge)




$C_{eq} = C_1 + C_2$   
 $Q_{1, initial} = C_{eq} \Delta V_f = Q_1 + Q_2$

$\Delta V_f = \frac{Q_{1, initial}}{C_{eq}} = \frac{C_1 \Delta V}{C_1 + C_2} = \boxed{10.3 \text{ Volt}}$


$Q_1 = C_1 \Delta V_f = \boxed{82.8 \mu C}$   
 $Q_2 = C_2 \Delta V_f = \boxed{93.2 \mu C}$

} NOTE  
 $Q_1 + Q_2 = Q_{1, initial} = 176 \mu C$

(10.)

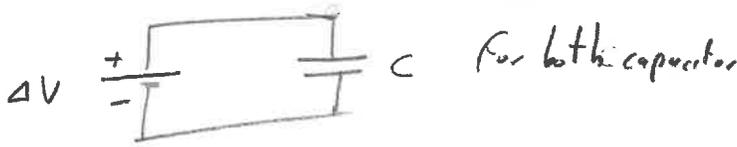


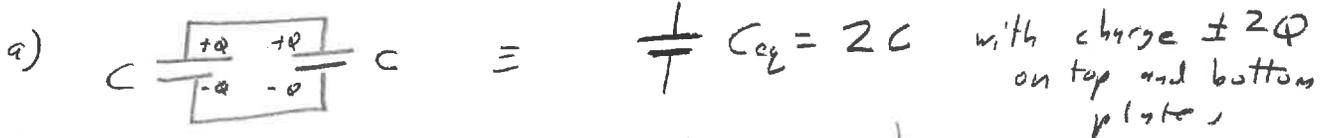$C = 15 \mu F$   
 $\Delta V = 45.5 \text{ Volt}$   
 $Q = C \Delta V$



$U_{initial} = \frac{1}{2} C_{eq} \Delta V^2 = 2 \left( \frac{1}{2} C \Delta V^2 \right)$   
 $= 15 \mu F (45.5 \text{ volt})^2$   
 $= \boxed{0.031 J}$

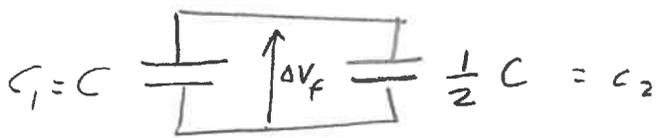b) plate separation in 1 capacitor is doubled  $\left( C = \frac{\epsilon_0 A}{d} \right)$



$2Q = Q_1 + Q_2$   
 $= C_1 \Delta V_f + C_2 \Delta V_f$   
 $= (C + \frac{1}{2} C) \Delta V_f$   
 $= \frac{3}{2} C \Delta V_f$

$\rightarrow \Delta V_f = \frac{4}{3} \frac{Q}{C} = \frac{4}{3} \Delta V = \boxed{60.66 \text{ Volt}}$

c) Total energy after doubling

$$\begin{aligned}U_{\text{final}} &= \frac{1}{2} \left( \frac{3}{2} C \right) \Delta V^2 \\&= \frac{3}{4} C \left( \frac{4}{3} \Delta V \right)^2 \\&= \frac{4}{3} C \Delta V^2 \\&= \frac{4}{3} U_{\text{initial}} \\&= \boxed{0.041 \text{ Joule}} > U_{\text{initial}}\end{aligned}$$

d) Positive work done by agent pulling plates apart

⑪ Teflon filled:  $k = 2$

$$a) \text{ Area} = 1.70 \text{ cm}^2 \times \left( \frac{10^{-4} \text{ m}^2}{\text{cm}^2} \right) = 1.70 \times 10^{-4} \text{ m}^2$$

$$d = 0.08 \text{ mm} = 0.08 \times 10^{-3} \text{ m}$$

$$\text{Parallel plate capacitor } C = \frac{k \epsilon_0 A}{d} = \boxed{37.6 \text{ pF}}$$

b) Maximum potential difference for teflon capacitor

Dielectric breakdown:  $30 - 60 \frac{\text{kV}}{\text{mm}}$  (for teflon)

$$E = \frac{|\Delta V|}{d} \rightarrow |\Delta V| = E d$$

$$\begin{aligned}\Delta V_{\text{max}} &= E_{\text{max}} d \\&= 30 \frac{\text{kV}}{\text{mm}} (0.08 \text{ mm}) \\&= \boxed{2.4 \text{ kV}}\end{aligned}$$